

## Module 2 Assignment

### 7nm FinFET Device and Inverter Characterization

**Name:** Indrani Aekabote

**Date:** 16<sup>th</sup> Dec '25

**SPICE file used:** inverter\_assign\_2.spice

**Sch file used:** inverter\_assign\_2.sch

**Extracting the following metrics from simulation results:**

- Switching Threshold Voltage (VTC) in mV
- Drain Current ( $I_d$ ) in  $\mu A$
- Power Consumption (P) in fW (femto watt)
- Propagation Delay ( $t_{pd}$ ) in ps
- Gain ( $A_v$ )
- Noise Margin (NM)
- Transconductance ( $g_m$ ) in  $10^{-3}$
- Frequency (f) in Hz

## Characterization Table:

CHARACTERIZATION TABLE

Trial no.	W (PMOS)	W (NMOS)	L (PMOS, NMOS)	W/L (PMOS)	W/L (NMOS)	V <sub>th</sub> (in mV)	I <sub>d</sub> (in uA)	Power (in fW)	t <sub>pd</sub> (in ps)	Gain / A <sub>v</sub>	freq. (in Hz)	Noise margin	Transconductance (gm) x 10 <sup>-3</sup>	O/p resistance (Ro)
1	14	14	7	2	2	344.79	226.07	-1.185	0.4495	6.4284	2.2247	NMH: -0.032019 NML: 0.044396	1.2358	6.428
2	10	14	7	1.4286	2	321.55	226.03	-1.425	0.4426	6.4812	2.2592	NMH: -0.025006 NML: 0.037397	0.96853	6.42842
3	11	14	7	1.5714	2	328.11	201.21	-1.049	0.4432	6.4572	2.2563	NMH: -0.026799 NML: 0.0394854	1.040534	6.457
4	12	14	7	1.7143	2	334.12	210.1	-1.098	0.4438	6.4424	2.2532	NMH: -0.028999 NML: 0.041478	1.108422	6.44233
5	13	14	7	1.8571	2	339.66	218.36	-1.143	0.4445	6.4324	2.2499	NMH: -0.030415 NML: 0.0430194	1.173429	6.43224
6	14	15	7	2	2.1429	340.01	234.52	-1.754	0.4451	6.4326	2.2496	NMH: -0.030590 NML: 0.0429329	1.26179	6.43263
7	13	16	7	1.8571	2.2857	330.42	233.84	-1.221	0.4434	6.4514	2.5515	NMH: -0.027690 NML: 0.0400151	1.218675	6.45133
8	14	17	7	2	2.4286	331.35	250.16	-1.306	0.4352	6.4489	2.2547	NMH: -0.028023 NML: 0.0403602	1.307588	6.44895
9	14	10	7	2	1.4286	367.95	186.75	-1.415	4.4955	6.4529	2.2244	NMH: -0.038091 NML: 0.0507028	1.10319	6.45263
10	14	13	7	2	1.8571	349.91	217.12	-1.141	4.4596	6.4273	2.2424	NMH: -0.032979 NML: 0.0455739	1.207359	6.42807
11	12	11	7	1.7143	1.5714	350.09	184.77	-1.388	4.461	6.4277	2.2416	NMH: -0.033175 NML: 0.0457869	1.030588	6.42762
12	17	13	7	2.4286	1.8571	363.28	236.12	-1.784	4.4849	6.4423	2.2297	NMH: -0.036622 NML: 0.0492198	1.373	6.4422
13	16	11	7	2.2857	1.5714	370.55	208.6	-1.583	4.5019	6.4594	2.2216	NMH: -0.038552 NML: 0.0515534	1.24307	6.45933
14	15	16	7	2.1429	2.2857	340.32	250.69	-1.313	4.4455	6.4318	2.2495	NMH: -0.030307 NML: 0.042819	1.350136	6.43193
15	15	12	7	2.1429	1.7143	360.18	213.86	-1.13	4.4784	6.4369	2.233	NMH: -0.036207 NML: 0.048733	1.23082	6.43688

## Ensuring Unique Results

Including the following trick in my SPICE deck, adding a dummy voltage source:

Vuniq in 0 DC <your\_username\_ASCII\_sum\_in\_mV>

Example: My username is Indrani,

➔ convert to ASCII (73+110+100+82+97+110+105 =677)

Using: Vuniq in 0 DC 0.677

[This introduces a small offset in simulation, making your result traceable and unique.]

## SPICE code:

```
** sch_path: /home/Desktop/asap_7nm_Xschem/inverter_assign_2.sch
**.subckt inverter_assign_2
Xpfet1 nfet_out nfet_in vdd vdd asap_7nm_pfet l=7e-009 nfin=14
Xnfet1 nfet_out nfet_in GND GND asap_7nm_nfet l=7e-009 nfin=14
V1 nfet_in GND pulse(0 0.7 20p 10p 10p 20p 500p 1)
V2 vdd GND 0.7
Vuniqu in 0 DC 0.677

**** begin user architecture code
*.dc v1 0 0.7 1m
*.tran 1e-12 100e-12

.control
  * First run DC
  dc v1 0 0.7 1m
  run
  * DC measurements
  meas dc v_th when nfet_out = nfet_in
  plot nfet_out nfet_in

  let gain_av = abs(deriv(nfet_out))
  meas dc max_gain max gain_av
  let gain_target = max_gain * 0.999
  meas dc vil find nfet_in when gain_av = gain_target cross=1
  meas dc voh find nfet_out when gain_av = gain_target cross=1
  meas dc vih find nfet_in when gain_av = gain_target cross=2
  meas dc vol find nfet_out when gain_av = gain_target cross=2
  let nmh = voh - vih
  let nml = vil - vol
  print v_th max_gain vil voh vih vol nmh nml

  *Transconductance

  let id = v2#branch
  let gm = real(deriv(id, nfet_in))
  meas dc gm_max MAX gm
  plot gm
  let r_out= deriv(nfet_out,id)
  let abs_rout= abs(r_out)
  meas dc max_r_out max abs_rout
  print max_r_out
  plot r_out
```

plot id

\* Transient measurements

tran 1e-12 100e-12

meas tran tpr when nfet\_in = 0.35 rise = 1

meas tran tpf when nfet\_out = 0.35 fall = 1

let tp = (tpr + tpf) / 2

let trans\_current = v2#branch

meas tran id\_pwr integ trans\_current from=2e-11 to=6e-11

let pwr = id\_pwr \* 0.7

let power = abs(pwr / 4e-11)

print tpr tpf tp id\_pwr pwr power

tran 0.1 100p

meas tran tr when nfet\_in=0.07 RISE=1

meas tran tf when nfet\_out=0.63 FALL=1

let t\_delay = tr + tf

print t\_delay

let f = 1/t\_delay

print f

.endc

\*\*\*\* end user architecture code

\*\*.ends

.GLOBAL GND

\*\*\*\* begin user architecture code

.subckt asap\_7nm\_pfet S G D B l=7e-009 nfin=15

    npmos\_finfet S G D B BSIMCMG\_osdi\_P l=7e-009 nfin=15

.ends asap\_7nm\_pfet

.model BSIMCMG\_osdi\_P BSIMCMG\_va (

+ TYPE = 0

\*\*\*\*\*

\*                    general                    \*

\*\*\*\*\*

+version = 107            bulkmod = 1            igcmod = 1            igbmod = 0

+gidlmod = 1            iiimod = 0            geomod = 1            rdsmod = 0

+rgatemod = 0            rgeomod = 0            shmod = 0            nqsmod = 0

+coremod = 0            cgeomod = 0            capmod = 0            tnom = 25

+eot = 1e-009 eotbox = 1.4e-007 eotacc = 3e-010 tfin = 6.5e-009  
+toxp = 2.1e-009 nbody = 1e+022 phig = 4.9278 epsrox = 3.9  
+epsrsub = 11.9 easub = 4.05 ni0sub = 1.1e+016 bg0sub = 1.17  
+nc0sub = 2.86e+025 nsd = 2e+026 ngate = 0 nseg = 5  
+l = 2.1e-008 xl = 1e-009 lint = -2.5e-009 dlc = 0  
+dlbin = 0 hfin = 3.2e-008 deltaw = 0 deltawcv = 0  
+sdterm = 0 epsrsp = 3.9 nfin = 1  
+toxg = 1.8e-009

\*\*\*\*\*

\* dc \*

\*\*\*\*\*

+cit = 0 cdsc = 0.003469 cdscd = 0.001486 dvt0 = 0.05  
+dvt1 = 0.36 phin = 0.05 eta0 = 0.094 dsub = 0.24  
+k1rsce = 0 lpe0 = 0 dvtshift = 0 qmfactor = 0  
+etaqm = 0.54 qm0 = 2.183e-012 pqm = 0.66 u0 = 0.0237  
+etamob = 4 up = 0 ua = 1.133 eu = 0.05  
+ud = 0.0105 ucs = 0.2672 rdswwmin = 0 rdsww = 200  
+wr = 1 rswmin = 0 rdwwmin = 0 rshs = 0  
+rshd = 0 vsat = 60000 deltavsat = 0.17 ksativ = 1.592  
+mexp = 2.491 ptwg = 25 pclm = 0.01 pclmg = 1  
+pdibl1 = 800 pdibl2 = 0.005704 drout = 4.97 pvag = 200  
+fpitch = 2.7e-008 rth0 = 0.15 cth0 = 1.243e-006 wth0 = 2.6e-007  
+lcdscd = 0 lcdscdr = 0 lrdsw = 1.3 lvsat = 1441

\*\*\*\*\*

\* leakage \*

\*\*\*\*\*

+aigc = 0.007 bigc = 0.0015 cigc = 1 dlcigs = 5e-009  
+dlcigd = 5e-009 aigs = 0.006 aigd = 0.006 bigs = 0.001944  
+bigd = 0.001944 cigs = 1 cigd = 1 poxedg = 1.152  
+agidl = 2e-012 agisl = 2e-012 bgidl = 1.5e+008 bgisl = 1.5e+008  
+egidl = 1.142 egisl = 1.142

\*\*\*\*\*

\* rf \*

\*\*\*\*\*

\*\*\*\*\*

\* junction \*

\*\*\*\*\*

\*\*\*\*\*

\* capacitance \*

\*\*\*\*\*

+cfs = 0 cfd = 0 cgso = 1.6e-010 cgdo = 1.6e-010  
+cgsl = 0 cgdl = 0 ckappas = 0.6 ckappad = 0.6  
+cgbo = 0 cgbl = 0

\*\*\*\*\*

\* temperature \*

```

*****
+tbgasub = 0.000473    tbgbsub = 636      kt1   = 0      kt1l  = 0
+ute   = -1.2        utl   = 0          ua1   = 0.001032    ud1   = 0
+ucste  = -0.004775    at    = 0.001      ptwgt  = 0.004      tmexp  = 0
+prt   = 0           tgidl  = -0.007      igt    = 2.5
*****
*                   *
*****

**)
.control
pre_osdi /home/vsduser/Desktop/asap_7nm_Xschem/bsimcmg.osdi
.endc


.subckt asap_7nm_nfet S G D B l=7e-009 nfin=12
    nnmos_nfet S G D B BSIMCMG_osdi_N l=7e-009 nfin=12
.ends asap_7nm_nfet


.model BSIMCMG_osdi_N BSIMCMG_va (
+ TYPE = 1
*****
*                   *
*****

+version = 107      bulkmod = 1      igcmod = 1      igbmod = 0
+gidlmod = 1        iimod  = 0      geomod = 1      rdsmod = 0
+rgatemod= 0        rgeomod = 0      shmod  = 0      nqsmode = 0
+coremod = 0        cgeomod = 0      capmod = 0      tnom   = 25
+eot   = 1e-009     eotbox = 1.4e-007    eotacc = 1e-010    tfin   = 6.5e-009
+toxp  = 2.1e-009   nbody  = 1e+022     phig   = 4.2466    epsrox = 3.9
+epsrsub = 11.9     easub  = 4.05      ni0sub = 1.1e+016   bg0sub = 1.17
+nc0sub = 2.86e+025 nsd    = 2e+026      ngate  = 0         nseg   = 5
+l     = 2.1e-008   xl     = 1e-009     lint   = -2e-009   dlc    = 0
+dlbin = 0          hfin   = 3.2e-008    deltaw = 0         deltawcv= 0
+sdterm = 0         epsrsp = 3.9         nfin   = 1
+toxg  = 1.80e-009
*****
*                   *
*****

+cit   = 0          cdsc  = 0.01      cdsd   = 0.01      dvt0   = 0.05
+dvt1  = 0.47       phin  = 0.05      eta0   = 0.07      dsub   = 0.35
+k1rsce = 0         lpe0  = 0          dvtshift= 0        qmfactor= 2.5
+etaqm  = 0.54      qm0   = 0.001     pqm    = 0.66      u0     = 0.0303
+etamob = 2         up    = 0          ua     = 0.55      eu     = 1.2
+ud     = 0         ucs   = 1          rdswmin = 0        rdsw   = 200

```

```

+wr    = 1          rswmin = 0          rdwmin = 0          rshs  = 0
+rshd   = 0          vsat   = 70000      deltavsat= 0.2        ksativ = 2
+mexp   = 4          ptwg   = 30         pclm   = 0.05        pclmg  = 0
+pdibl1 = 0          pdibl2 = 0.002      drout   = 1          pvag   = 0
+fpitch = 2.7e-008   rth0    = 0.225     cth0    = 1.243e-006   wth0   = 2.6e-007
+lcdscd = 5e-005      lcdscdr = 5e-005    lrdsw   = 0.2         lvsat  = 0

```

```

*****

```

```

*                leakage                *

```

```

*****

```

```

+aigc   = 0.014      bigc   = 0.005      cigc   = 0.25        dlcigs = 1e-009
+dlcigd = 1e-009     aigs   = 0.0115     aigd   = 0.0115     bigs   = 0.00332
+bigd   = 0.00332    cigs   = 0.35       cigd   = 0.35       poxedge = 1.1
+agidl  = 1e-012     agisl  = 1e-012     bgidl  = 10000000    bgisl  = 10000000
+egidl  = 0.35       egisl  = 0.35

```

```

*****

```

```

*                rf                *

```

```

*****

```

```

*****

```

```

*                junction            *

```

```

*****

```

```

*****

```

```

*                capacitance        *

```

```

*****

```

```

+cfs    = 0          cfd    = 0          cgso   = 1.6e-010    cgdo   = 1.6e-010
+cgsi   = 0          cgdi   = 0          ckappas = 0.6       ckappad = 0.6
+cgbo   = 0          cgbi   = 0

```

```

*****

```

```

*                temperature        *

```

```

*****

```

```

+tbgasub = 0.000473   tbgbsub = 636      kt1    = 0          kt1l   = 0
+ute     = -0.7        utl     = 0          ua1    = 0.001032    ud1    = 0
+ucste   = -0.004775   at      = 0.001     ptwgt   = 0.004     tmexp   = 0
+prt     = 0           tgidl   = -0.007     igt     = 2.5

```

```

*****

```

```

*                noise                *

```

```

*****

```

```

**)

```

```

.control

```

```

pre_osdi /home/vsduser/Desktop/asap_7nm_Xschem/bsimcmg.osdi

```

```

.endc

```

```

**** end user architecture code


```

```


.end

```
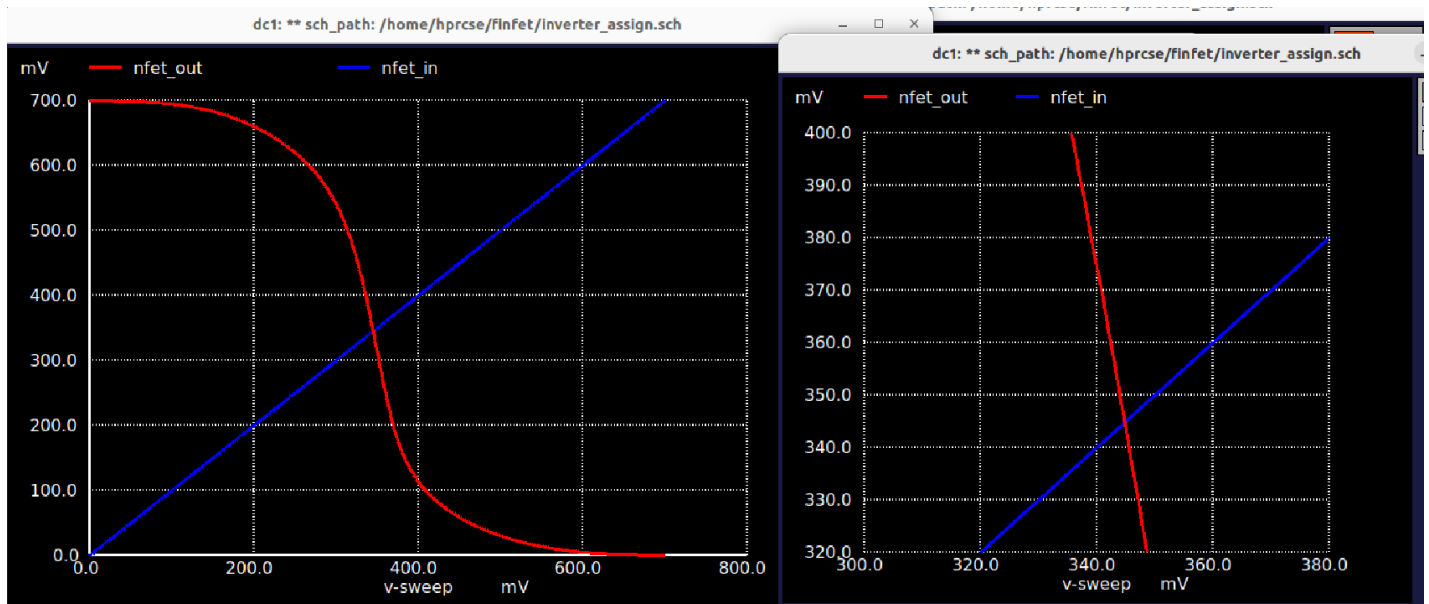
## Graphs of VTC, Delay and $I_D$ curves:




VTC Graph

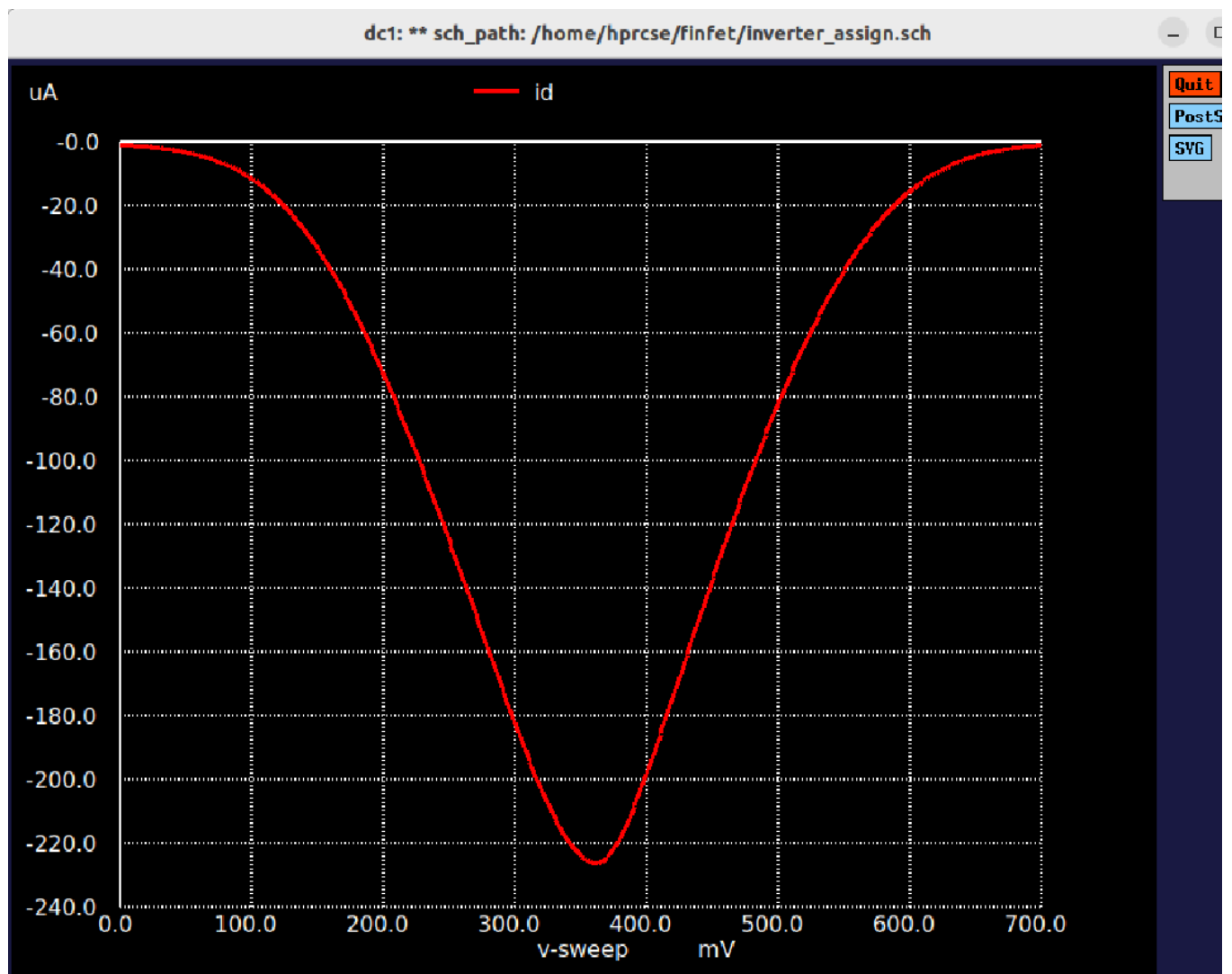


$I_D$  Curve




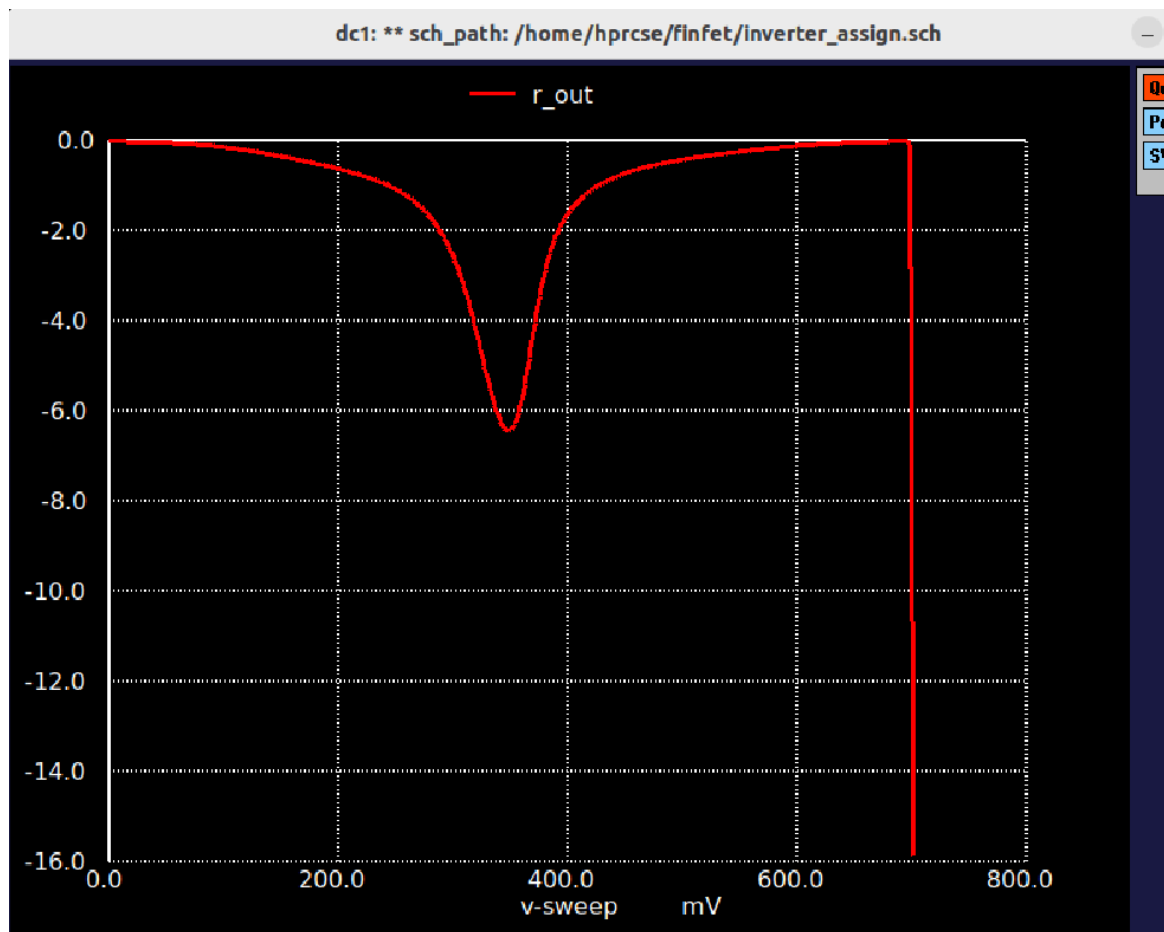

Output Resistance Graph ( $r_{out}$ )

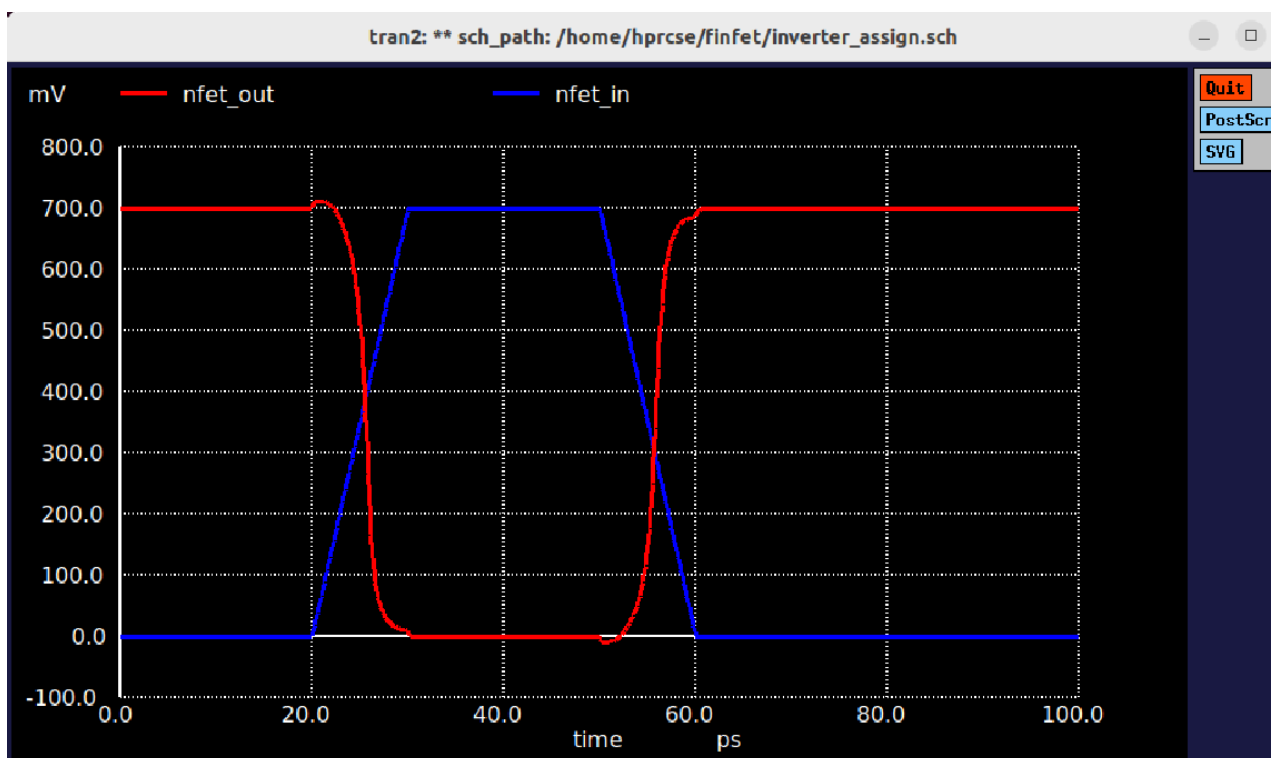

n-FET output and input plot

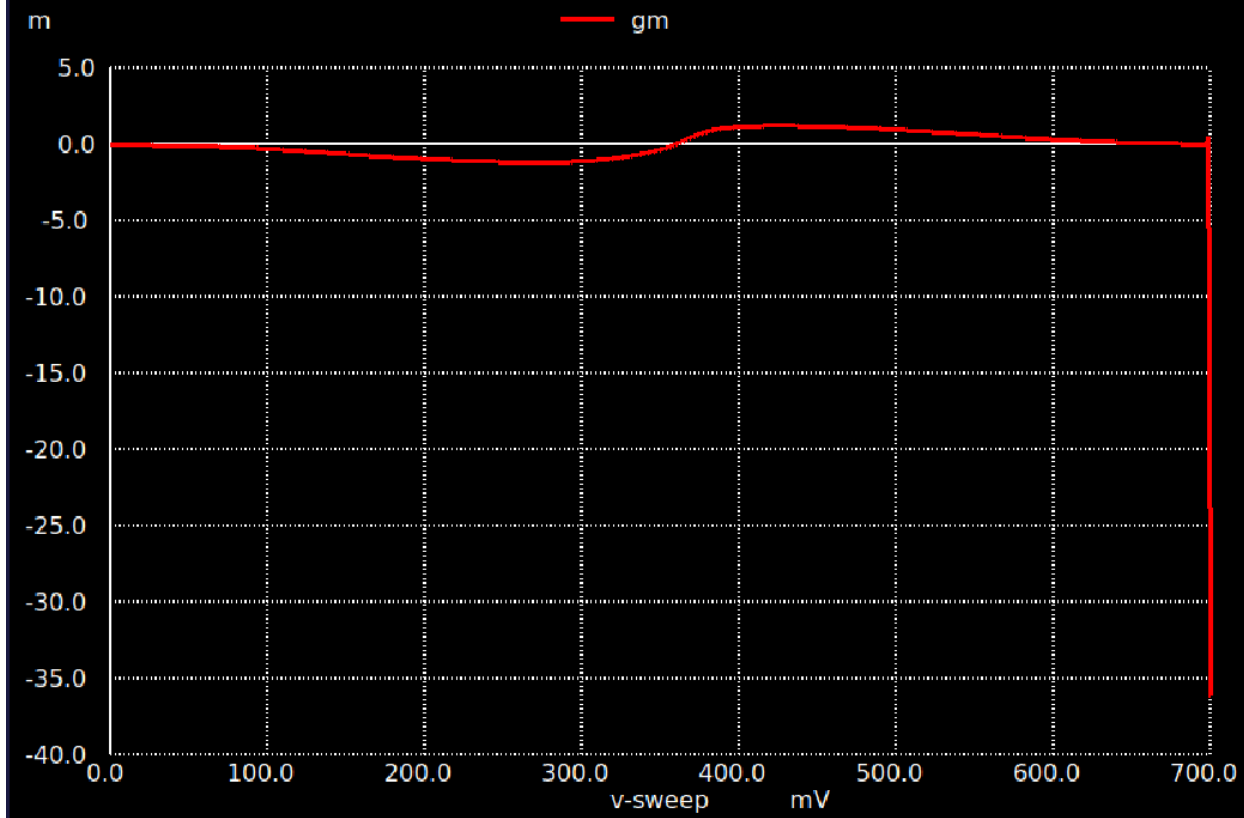

Transconductance (Gm) Curve